



An MoE Govt of India Initiative



## BJT- CE OUTPUT CHARACTERISTICS

### INSTRUCTION

#### EXPERIMENTAL TABLE

Serial No.	Base-Current 15.35 $\mu$ A	
	Collector-Emitter Voltage V	Collector Current mA
1	0.1000	5.994
2	0.8000	39.94
3	1.700	56.26
4	2.600	59.48
5	3.500	60.03
6	4.500	60.13
7	5.400	60.14
8	6.200	60.14
9	7.000	60.14
10	8.100	60.14


### CONTROLS

$R_{h1}$   Ohms 15  
 $R_{h2}$   Ohms 81

Add to Table


Plot

Clear

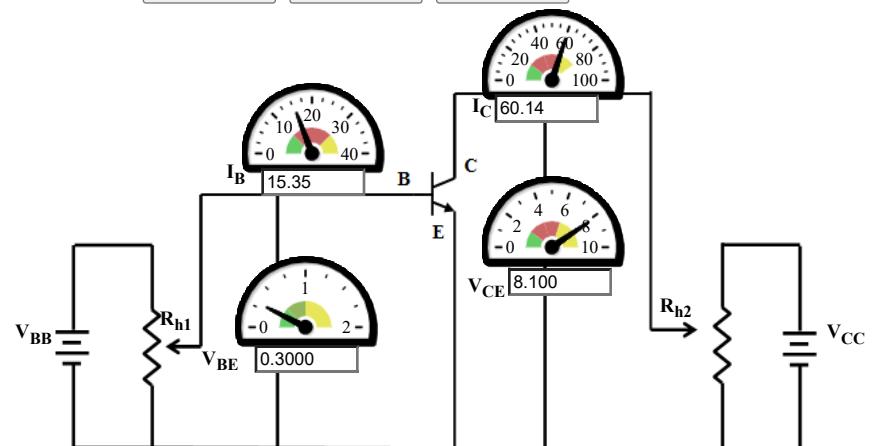

### GRAPH PLOT

V-I Plot

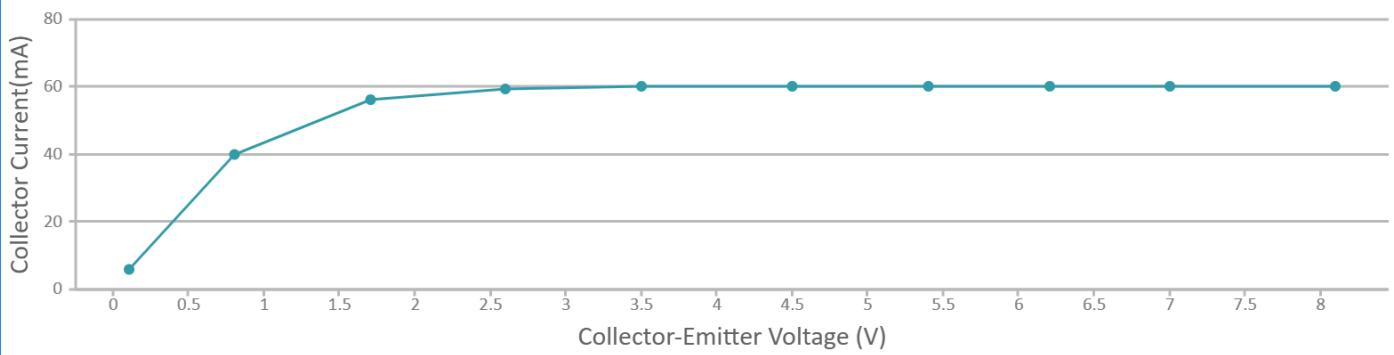  
Print


Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)